



**K. J. Somaiya College of Engineering, Mumbai-77**  
(A Constituent College of Somaiya Vidyavihar University)

Batch: A2 Roll No.: 16010322014

Experiment / assignment / tutorial No. 57

Grade: AA / AB / BB / BC / CC / CD / DD

Signature of the Staff In-charge with date 27/10/25

**TITLE:** Design of matching network for given load using lumped elements.

**AIM:** To Design lumped elements (L and C) matching network for given load using Open source "Smith simulation software".

**OUTCOME:** Analyse and design microwave transmission lines and matching circuits.

Example 1.

~~Design a single stub matching network for a load of  $120 + j35 \Omega$  load using single open circuit shunt stub.~~

~~Assume characteristic impedance of transmission line & stub as  $50 \Omega$ .~~

Example 2.

~~Design a matching network for microstrip antenna connected to coaxial cable whose characteristic impedance is  $50 \Omega$  input impedance for antenna is  $60 + j25 \Omega$~~

~~Design single stub using shunt short circuit stub.~~

Result:



Sr No.	Theoretical		Simulated	
	Type of element 1 and Value of element 1 From the load end	Type of element 2 and Value of element 2 From the load end	Type of element 1 and Value of element 1 From the load end	Type of element 2 and Value of element 2 From the load end
Example 1	Parallel capacitor 0.95pF	Series Inductor 38.9nH	Parallel capacitor 0.943pF	Series Inductor 38.7nH
Example 2	Series capacitor 15.9 pF	Parallel Inductor 3.98 nH	Series Capacitor 15.8pF	Parallel Inductor 4 nH

Signature of faculty in-charge

**Circuit diagram:**

Example 1

Example 2

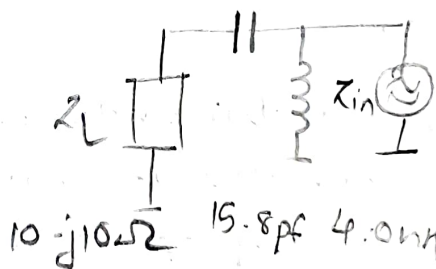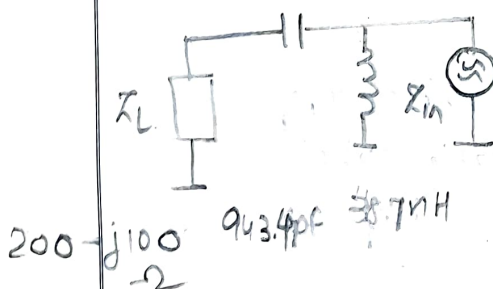

**Design by theoretical method:**

## Example 1

Design 1 section matching NLW to match series RC load with an impedance  $Z_L = (200 - j100) \Omega$  to a  $100 \Omega$  line at frequency of  $500 \text{ MHz}$

Nature of load  $\rightarrow$  series RC

$$Z_L = 200 - j100 \Omega$$

$$Z_0 = 100 \Omega$$

$$f = 500 \text{ MHz}$$

Normalized susceptance

$$b = \frac{B}{Y_0} = x_0$$

$$x = \frac{x}{Z_0} \rightarrow \text{Normalized reactance}$$

i)  $b$  is -ve  $L = \frac{Z_0}{2\pi f b}$

$b$  is +ve  $C = \frac{1}{2\pi f Z_0 b}$

$x$  is -ve  $C = \frac{1}{2\pi f x Z_0}$

$x$  is +ve  $L = \frac{2Z_0}{2\pi f x}$

$$Z_L' = \frac{200 - j100}{100}$$

$$= 2 - j1$$

v)  $Z_L = R - jX_C$   
 $R = 200 \Omega$   
 $X_C = 100$

$$y_d = 0.4 + j0.5 \quad \frac{1}{2\pi f C} = 100$$



$$jB = y_d - y_L$$

$$= j0.3$$

$$C = 3.18 \text{ pF}$$

$$C = \frac{B}{2\pi f Z_0} = \frac{0.3}{2\pi (500 \times 10^6) \times 100}$$

$$= 0.95 \text{ pF}$$

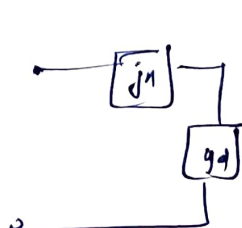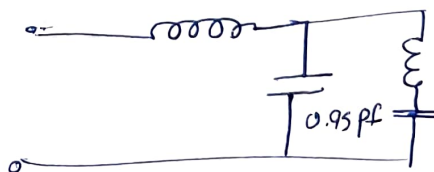



$$Z_d = 1 - j1.2$$

$$jB = j1.2$$

$$L = \frac{2Z_0}{2\pi f} = 38.2 \text{ nH}$$

ii)  $K_L = 2 - j1$

iii)  $1 + j2$ , inside the circle

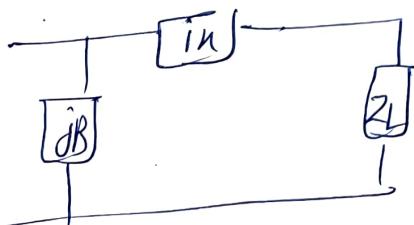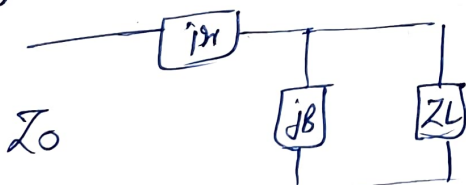

$$y_L = 0.4 + j0.2$$

iv) \*

## Example 2

Design lumped element matching n/w for


$$Z_L = 10 - j10 \Omega$$

$$Z_0 = 50 \Omega$$

$$f = 1 \text{ GHz}$$

$$\begin{aligned} Z_L' &= \frac{Z_L}{Z_0} = \frac{10 - j10 \Omega}{50 \Omega} \\ &= 0.2 - j0.2 \end{aligned}$$

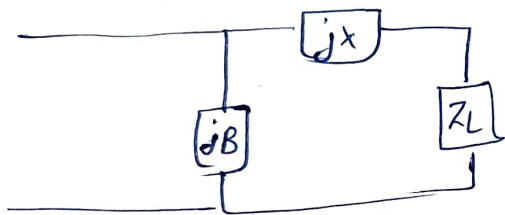Since,  $Z_L'$  lies outside circle, hence matching ckt can be drawn  $\rightarrow$



$$Z_d = jx + \bar{Z}_L$$

$$\begin{aligned} Z_d &= jx + Z_L \quad (1 + j\beta \text{ circle}) \\ &= 0.2 - 0.4 \\ &= -j0.2 \end{aligned}$$

$$b \text{ is -ve} \rightarrow L = \frac{Z_0}{2\pi f_0}$$

$$b \text{ is +ve} \rightarrow C = \frac{b}{2\pi f Z_0}$$

$$x \text{ is -ve} \rightarrow C = \frac{1}{2\pi f_n Z_0}$$

$$x \text{ is +ve} \rightarrow L = \frac{x Z_0}{2\pi f}$$

$$y_d = 1 + j2$$

$$j\beta + y_d = 1$$

$$j\beta = 1 - y_d$$

$$= 1 - 1 - j2$$

$$j\beta = -j2$$


$$\begin{aligned} C &= \frac{1}{2\pi} \times \frac{1}{10^9} \times \frac{1}{0.2 \times 50} \\ &= 15.9 \text{ pF} \end{aligned}$$

$$L = \frac{Z_0}{2\pi f_0} = \frac{50}{2\pi \times 10^9 \times 2}$$


$$= 3.98 \text{ nH}$$



Ex 1

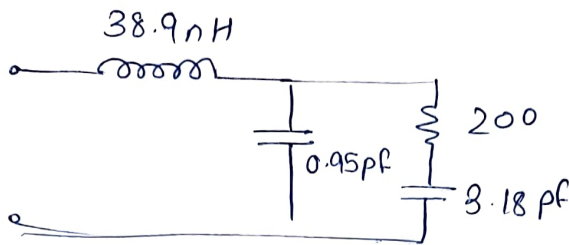

Ex 2

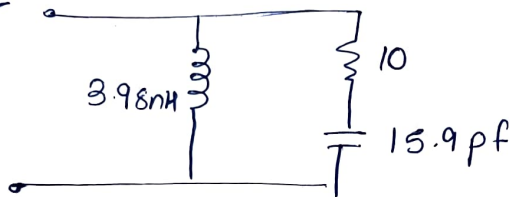


**Conclusion:**


(Compare results by Smith chart method and Simulation)

In this experiment, we have designed lumped elements (L and C) matching network for given load using open source "Smith simulation Software" and also verified the results theoretically. It has been observed that there was a slight change in the results after simulation in software as compared to theoretical calculations but they are close enough.

Q1

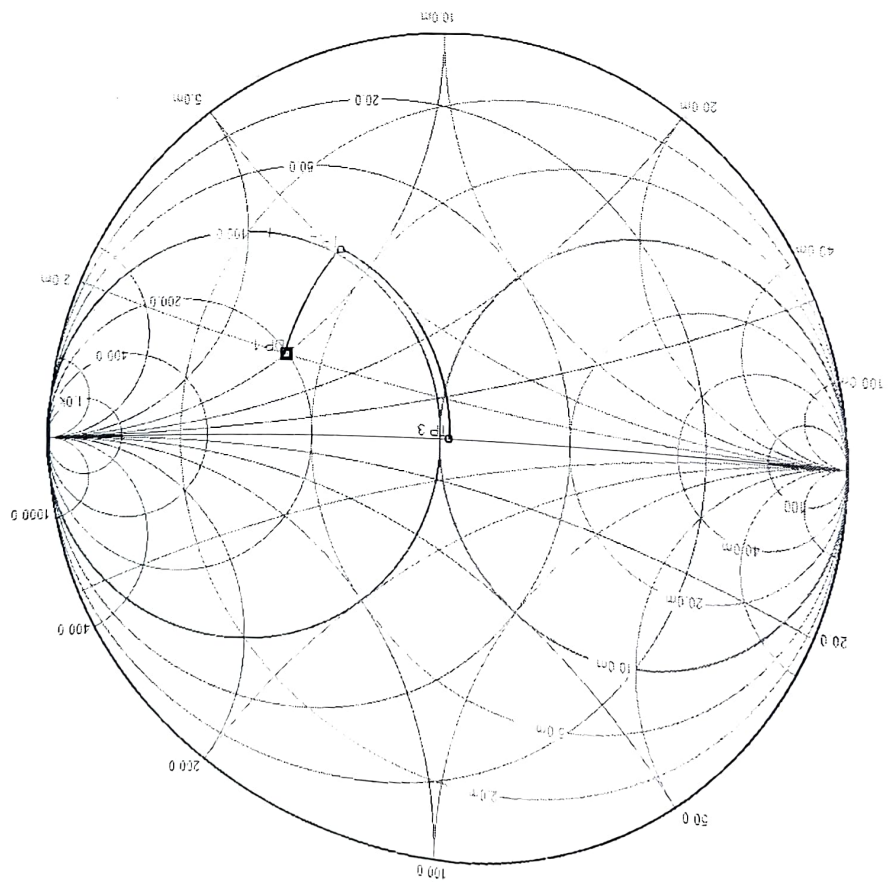

Schematic

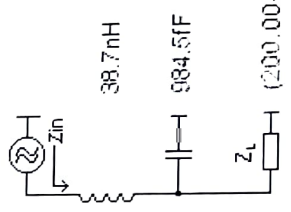


$(200.00 - j100.00) @ 500.00 \text{ MHz}$


Start DP	Point	Z	Q	Frequency
DP 1	(200.000 - j100.000)	Q = -0.500	500.000MHz	
TP 2	(95.380 - j121.440)	Q = -1.273	500.000MHz	
TP 3	(95.380 - j30.000)	Q = -0.000	500.000MHz	

Datapoints

Q2

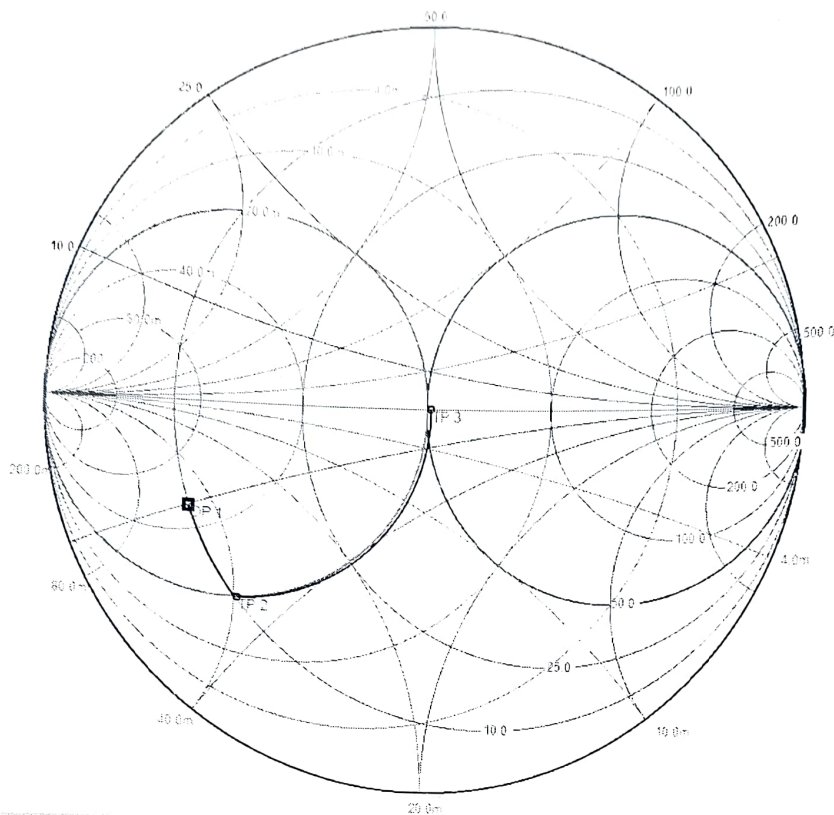

Schematic

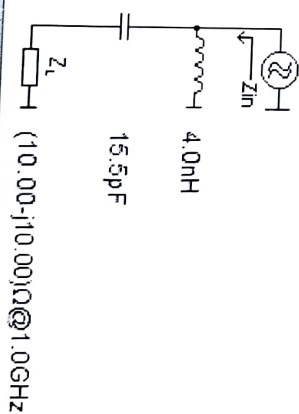

Data points

Start DP	Point	Z	Q	Frequency
<input checked="" type="checkbox"/>	TP 1	$(10.000 - j10.000) \Omega$	$Q=1.000$	1.000GHz
	TP 2	$(10.000 - j20.275) \Omega$	$Q=2.027$	1.000GHz
	TP 3	$(51.105 + j0.282) \Omega$	$Q=0.005$	1.000GHz