

Batch: A2 Roll No.: 16010322014
Experiment / assignment / tutorial No. 90
Grade: AA / AB / BB / BC / CC / CD / DD

Signature of the Staff In-charge with date
Date: 25/11/25

TITLE: Design of Microwave amplifier for the specified gain and its matching circuit.

AIM: To design Microwave amplifier for the specified gain using MATLAB/Smith software

OUTCOME: Design microwave amplifiers.

Parameters

Design an amplifier to have a gain of 11 dB at 4.0 GHz. Plot constant gain circles for $G_{IS} = 2 \text{ dB}$ and 3 dB , and $G_{IL} = 0 \text{ dB}$ and 1 dB . Calculate and plot the input return loss & overall amplifier gain from 3 to 5 GHz. The FET has the following S parameters ($Z_0 = 50 \Omega$)

$f(\text{GHz})$	S_{11}	S_{21}	S_{12}	S_{22}
3	$0.80 L - 90^\circ$	$2.8 L 100^\circ$	0	$0.66 L - 50^\circ$
-4	$0.75 L - 120^\circ$	$2.5 L 80^\circ$	0	$0.60 L - 70^\circ$
5	$0.71 L - 140^\circ$	$2.3 L 60^\circ$	0	$0.58 L - 85^\circ$

Stepwise-Procedure:

Using MATLAB commands or using Smith software

1. Input the s parameter for the given BJT/FET
2. Input frequency of operation
3. Input the specified gain in dB.
4. Check the stability condition for the given amplifier
5. Calculate $G_{S\max}$, $G_{L\max}$, G_0 in dB.
6. Calculate FTUmax
7. For I/P side or source calculate the parameters of I/p gain circles.
8. For O/P or Load calculate the parameter of O/P gain circles.
9. Plot I/P & O/P gain circles on the smith chart

Theoretical Calculations:
Complete theoretical design of amplifier:

Since $S_{12} = 0$ and $|S_{11}| < 1$ and $|S_{22}| < 1$, the transistor is unilateral and unconditionally stable. From (11.47) we calculate the maximum matching section gains as

$$G_{S\max} = \frac{1}{1 - |S_{11}|^2} = 2.29 = 8.6 \text{ dB}$$

$$G_{L\max} = \frac{1}{1 - |S_{22}|^2} = 1.56 = 1.9 \text{ dB}$$

Gain of the mismatched transistor is

$$G_0 = |S_{21}|^2 = 6.25 \cancel{+ 8.0 \text{ dB}} = 7.95 \text{ dB} \approx 8.0 \text{ dB}$$

So the max. unilateral transducer gain is

$$G_{TU\max} = 8.6 + 1.9 + 8.0 = 18.5 \text{ dB}$$

$$G_S = 3 \text{ dB} \quad g_s = 0.875$$

$$C_S = 0.706 \angle 120^\circ \quad R_S = 0.166 \Omega$$

$$G_{S'} = 2 \text{ dB}$$

$$g_s = 0.691$$

$$C_S = 0.627 \angle 120^\circ \quad R_S = 0.294 \Omega$$

$$G_{L'} = 1 \text{ dB}$$

$$g_L = 0.806$$

$$C_L = 0.520 \angle 70^\circ \quad R_L = 0.303 \Omega$$

$$G_L = 0 \text{ dB}$$

$$g_L = 0.640$$

$$C_L = 0.440 \angle 70^\circ \quad R_L = 0.440 \Omega$$

$G_S = 2 \text{ dB}$ & $G_L = 1 \text{ dB}$, for overall amplifier gain of 11 dB.

Comparison of key amplifier design parameters:

Simulated	Theoretical
Transistor gain $G_0 = 8.0 \text{ dB}$	8.0 dB
I/P Gain $GS_{\max} = 3.6 \text{ dB}$ $G_{\max} = 13.46$	3.6 dB 13.5 dB
Reflection coefficient at I/P $= \Gamma_S$ $0.375 e^{j122^\circ}$	$0.34 e^{j120^\circ}$
Reflection coefficient at O/P $T_L = \Gamma_L$ $0.228 e^{j72^\circ}$ $0.229 e^{j71^\circ}$	$0.22 e^{j70^\circ}$

Conclusion:

Comment on the selection of Γ_S and Γ_L

In this experiment, a microwave amplifier was designed to achieve a specific gain of 8.0 dB at frequency. The amplifier parameters, such as the reflection coefficient at the input and output (Γ_S and Γ_L), were calculated & plotted using MATLAB or Smith software. The i/p & o/p gain circles were also analyzed to understand the amplifier's performance.


The selection of (Γ_S & Γ_L) played a crucial role in maximizing the gain & maintaining the stability of the amplifier. The practical transistor gain achieved was approximately 8.0 dB , which closely aligns with theoretical predictions.

This demonstrates that the amplifier design methodology effectively met the design specifications, validating the procedure and theoretical calculations for microwave amplifier design.

Signature of faculty in-charge

* Post Lab Subjective Questions

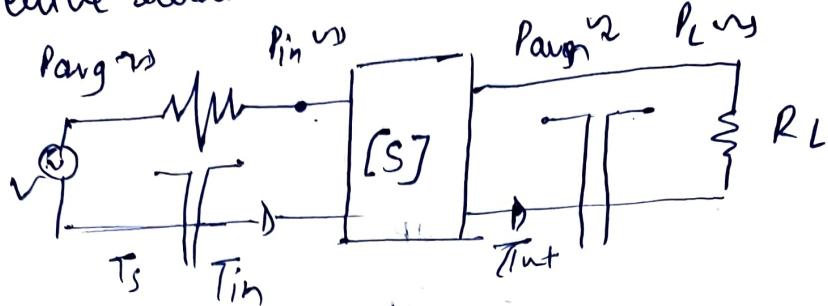1. Derive relation for transducer power gain of an



P_{ava} : power available from source

P_L : power deliverable to load

P_{in} : Power input

P_{out} : power available from new

Transducer power gain $G_T = P_L / P_{ava}$

Available power gain $G_A = P_{ava} / P_{ava}$

Operating power gain $G_p = P_L / P_{in}$

Conjugate matching $\rightarrow P_{in} = P_{ava}$ when $f_{in} = \sqrt{S}$

$$P_{ava} = P_L \quad f_{out} = \sqrt{L}$$

$$G_T = G_A = G_p \text{ when } f_{in} = \sqrt{S} \text{ & } f_{out} = \sqrt{L}$$

Transducer power gain G_T derivation

$$G_T = \frac{P_L}{P_{ava}}$$

So, power derived from load


$$P_L = \frac{1}{2} |b_2|^2 - \frac{1}{2} |a_2|^2 = \frac{1}{2} [b_2^2 - a_2^2], \text{ we know}$$

$$\text{that, } \Gamma_L = \frac{a_2}{b_2} \Rightarrow a_2 = \Gamma b_2 \quad P_L = \frac{1}{2} [b_2^2 (1 - \Gamma_L^2)] - (1)$$

relation for radius and center of constant gain at input and output section.

as available at source

$$P_{in} = P_{in}^+ - P_{in}^- = \frac{1}{2}|a_1|^2 - \frac{1}{2}|b_1|^2 \rightarrow (1)$$

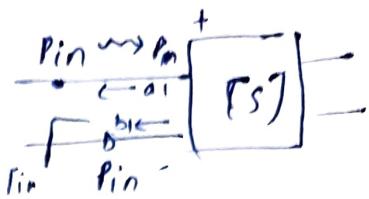

We know that $\Gamma_{in} = b_1/a_1$


$$P_{in} = \frac{1}{2}|a_1|^2 (1 - \Gamma_{in})^2 \rightarrow (2)$$

$P_{in} = P_{aus}$ when $\Gamma_{in} = \Gamma_S$

$$\therefore P_{aus} = \frac{1}{2}|a_1|^2 (1 - (\Gamma_S)^2)$$

$$G_{IT} = \frac{P_L}{P_{aus}} = \frac{|b_2|^2}{|b_1|^2} [1 - \Gamma_L] \rightarrow (3)$$

Signal flow graph:

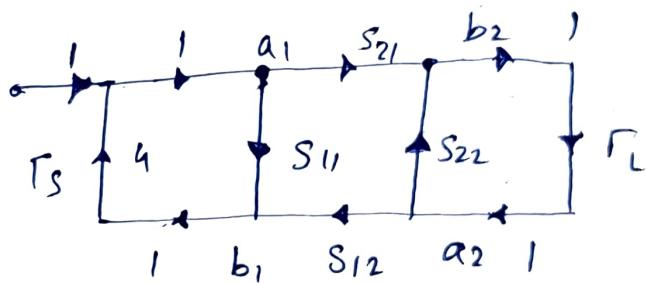

Mason's gain formula:

$$\frac{b_2}{b_1} = \frac{\gamma_1 \Delta_1}{A} = \frac{s_2}{1 - (s_{11}\Gamma_S + s_{22}\Gamma_L + s_{12}s_{21}\Gamma_S\Gamma_L) + (s_{11}\Gamma_S s_{22}\Gamma_L)}$$

Putting value in eq(3)


$$G_{IT} = \frac{|s_{21}|^2 (1 - \Gamma_L)^2 (1 - \Gamma_S)^2}{((1 - s_{22}\Gamma_L)(1 - \Gamma_S\Gamma_{in}))^2}$$

$$G_{IT} = \left[\frac{1 - \Gamma_S^2}{(1 - \Gamma_{in}\Gamma_S)^2} \right] \left[\frac{|s_{21}|^2}{G_o} \right] \left[\frac{1 - |\Gamma_L|^2}{|1 - s_{22}\Gamma_L|^2} \right]$$

$$G_{IT} = G_{IS} \cdot G_o \cdot G_L \quad \text{defined}$$

The Complete Smith Chart

Black Magic Design

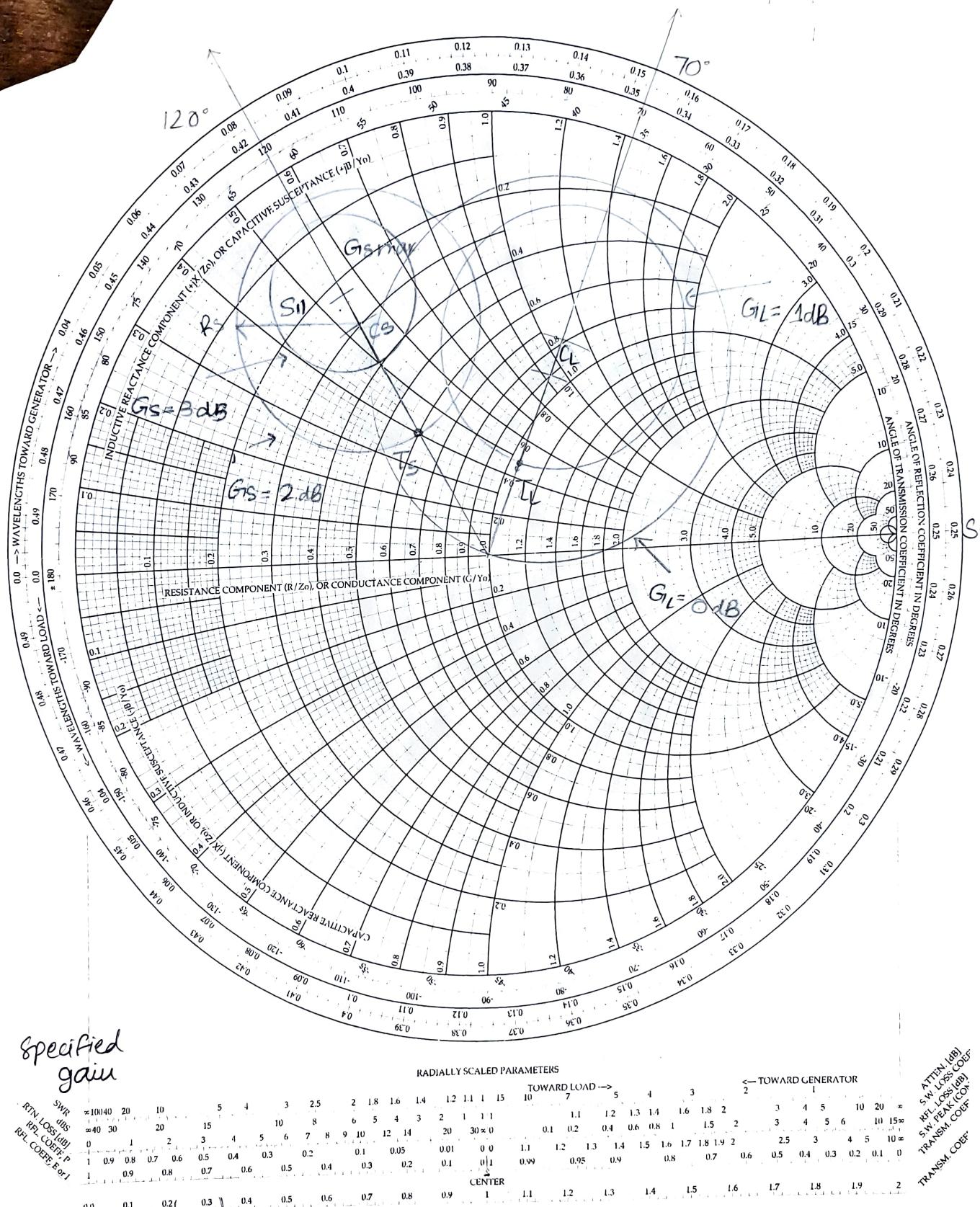

Specified
gain

RADIALY SCALED PARAMETERS

TOWARD LOAD \rightarrow 5 4 3 2 1 1 1 10 7 5 4 3 2 1 1 1 1.1 1.2 1.3 1.4 1.6 1.8 2 3 4 5 6 10 20

\leftarrow TOWARD GENERATOR 2 1 3 4 5 6 10 20

CENTER

SWR
REFL. COEF., R_L , P_{RL} , P_{SL}

ORIGIN

T_L

T_S

$0.22 \angle 70^\circ$ $0.34 \angle 20^\circ$

ATTEN. (dB)
REFL. LOSS (dB)
TRANSM. COEF. (CON.)
TRANSM. COEF. (OR)

1dB

$$C_L = 0.520$$

$$R_L = 0.303$$

0dB

$$C_L = 0.440$$

$$R_L = 0.440$$

2dB

$$C_S = 0.627$$

$$R_S = 0.294$$

3dB

$$C_S = 0.706$$

$$R_S = 0.166$$

$$\text{L} = 1 \text{ dB}$$

$$10 \log_{10} (G_L) = 1$$

$$\log_{10} (G_L) = 0.1$$

$$G_L = 10^{0.1}$$

$$G_L = 1.258 \\ \approx 1.26$$

$$g_L = \frac{G_L}{G_{L\max}} = \frac{1.258}{1.56} = 0.8064$$

ii) $G_L = 0 \text{ dB}$ $\Rightarrow g_L = \frac{G_L}{G_{L\max}}$

$$10 \log_{10} (G_L) = 0$$

$$g_L = \frac{1}{1.56}$$

$$\log_{10} (G_L) = 0.3$$

$$g_L = 0.640$$

$$G_L = 10^\circ$$

$$G_L = 1$$

$$C_L = \frac{g_L S^*_{22}}{1 - (1-g_L) |S_{22}|^2}$$

$$R_L = \frac{\sqrt{1-g_L} (1-|S_{22}|^2)}{1 - (1-g_L) |S_{22}|^2}$$

1dB

$$C_L = \frac{(0.8064) 0.60L - 70^\circ}{1(1-0.8064) |0.60L - 70^\circ|^2}$$
$$= 0.520 L 70^\circ$$

0dB

$$C_L = \frac{(0.640) 0.60L - 70^\circ}{1(1-0.640) |0.60L - 70^\circ|^2}$$
$$= 0.440 L 70^\circ$$

1dB

$$R_L = \frac{\sqrt{1-0.8064} (1-|0.60L-70^\circ|^2)}{1-(1-0.8064) |0.60L-70^\circ|^2}$$
$$= 0.803$$

0dB

$$R_L = \frac{\sqrt{1-0.640} 0.60L - 70^\circ}{1(1-0.640) |0.60L - 70^\circ|^2}$$
$$= 0.440 \cancel{L 70^\circ}$$

$$G_S = 2 \text{ dB}$$

IV] $G_S = 3 \text{ dB}$

$$2 \text{ dB} = 10 \log_{10}(n)$$

$$3 \text{ dB} = 10 \log_{10}(n)$$

$$\frac{2}{10} = \cancel{\log_{10}(n)}$$

$$\frac{3}{10} = \log_{10}(n)$$

$$0.2 = \log_{10}(n)$$

$$0.3 = \log_{10}(n)$$

$$n = 10^{0.2}$$

$$n = 10^{0.3}$$

$$n = 1.584$$

$$n = 1.995$$

$$g_S = \frac{n}{G_S \max}$$

$$= \frac{1.584}{\cancel{3.6} 2.29}$$

$$\cancel{= 0.44} = 0.6917$$

$$g_S = \frac{n}{G_S \max}$$

$$= \frac{1.995}{\cancel{3.6} 2.29} = \cancel{0.554} 0.8711$$

$$c_S = \frac{g_S S_{11}^*}{1 - (1 - g_S) |S_{11}|^2}$$

$$r_S = \frac{\sqrt{1 - g_S} (1 - |S_{11}|^2)}{1 - (1 - g_S) |S_{11}|^2}$$

$$2 \text{ dB} = \frac{0.691 (0.75 L - 120^\circ)}{1 - (1 - 0.691) |0.75 L - 120^\circ|^2}$$

$$= 0.627 L 120^\circ$$

$$2 \text{ dB} = \frac{\sqrt{1 - 0.691} (1 - |0.75 L - 120^\circ|)^2}{1 - (1 - 0.691) |0.75 L - 120^\circ|^2}$$

$$= 0.294$$

$$3 \text{ dB} = \frac{0.871 (0.75 L - 120^\circ)}{1 - (1 - 0.871) |0.75 L - 120^\circ|^2}$$

$$= 0.706 L 120^\circ$$

$$3 \text{ dB} = \frac{\sqrt{1 - 0.871} (1 - |0.75 L - 120^\circ|)^2}{1 - (1 - 0.871) |0.75 L - 120^\circ|^2}$$

$$= 0.166$$

